

Arithmetic Circuits

C1: Adder

- ☐ Full Adder
- ☐ Carry-Ripple Adder
- ☐ Carry-Select Adder
- ☐ Carry-Lookahead Adder

C2: Multiplier


- ☐ Array Multiplier with CPA
- ☐ Array Multiplier with CSA

Single-Bit Addition

Half Adder

$$S = A \oplus B$$

$$C_{out} = A \cdot B$$

 


A	B	C_{out}	S
0	0		
0	1		
1	0		
1	1		

Full Adder

$$S = A \oplus B \oplus C$$
 
$$C_{out} = A \cdot B + A \cdot C + B \cdot C$$




A	B	C	C_{out}	S
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

Single-Bit Addition

Half Adder

$$S = A \oplus B$$

$$C_{out} = A \cdot B$$

 


A	B	C_{out}	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Full Adder

$$S = A \oplus B \oplus C$$
 
$$C_{out} = A \cdot B + A \cdot C + B \cdot C$$



A	B	C	C_{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


Anti-Symmetry

Full Adder Design I

- direct implementation from equations

$$S = A \oplus B \oplus C$$


$$C_{out} = MAJ(A, B, C)$$

 

Full Adder Design II

- Sum S as function of C_{out}
 
$$S = ABC + (A + B + C)\overline{(C_{out})}$$
- Notice: Pull-up path fully symmetric to pull-down path because of truth table anti-symmetry



Prof. Schumann

Digital System Design

83

Full Adder Design II

Characteristics

- Layout is uniform
- Transistor count is $24 + 2 \cdot INV$ only
- Carry-bit is faster than Sum: well suited for carry-ripple adders


Prof. Schumann

Digital System Design

84

Full Adder Design III

 - Dual-rail domino
 - Very fast, but large and power hungry
 - Used in very fast multipliers




Prof. Schumann

Digital System Design

85

N-bit Adders

 - Add two N-bit binary numbers
- N-bit adder also called Carry Propagate Adder
 - Each sum bit depends on all previous carries




Prof. Schumann

Digital System Design

86

Carry-Ripple Adder

 - Simplest design: cascade full adders
 - Critical path goes from C_{in} to C_{out}
 - Design full adder to have fast carry delay



Carry-Ripple Adder

- Propagation delay:

$$t_{carry-ripple} = (N - 1) \cdot t_c + t_s$$

t_c carry – delay of full adder


t_s sum – delay of full adder

Conclusion:

Design full adder with small carry-delay

Carry-Select Adder

 - For long word length carry-ripple adder is too slow
- Idea:
 - divide N-bit adder into K blocks
 - Each block needs two N/K-bit adders
 - each block precomputes the sum for both: $C_{in}=0$, $C_{in}=1$




Prof. Schumann

Digital System Design

89

Carry-Select Adder

 - When the precomputation is ready, the carry from the previous block is also ready, deciding which sum is correct
- The correct carry-out of each block is getting calculated by an AND+OR-Gate!




Prof. Schumann

Digital System Design

90

Carry-Select Adder

 

- Propagation delay for N-bit addition:

$$t_{carry-select} \approx t_{N/K-bit_Adder} + (K - 1) \cdot t_{AND+OR}$$

K number of blocks

Carry-Lookahead Adder

- Carry-lookahead adder computes the carry-bit for each bit position out of the input signals A_i, B_i, C_0 , $i=0 \dots N-1$
- Using intermediate signals: G(generate), P(propagate)

$$G_i = A_i \cdot B_i$$

$$P_i = A_i \oplus B_i$$

- It holds for each bit position

$$S = A \oplus B \oplus C_{in}$$

$$S = P \oplus C_{in}$$

$$C_{out} = A \cdot B + C_{in} \cdot (A + B)$$

$$C_{out} = G + C_{in} \cdot P$$

Carry-Lookahead Adder

1. step: Calculate bitwise Propagate und Generate
Bitwise PG Logic

$$P_0 = A_0 \oplus B_0 \quad G_0 = A_0 \cdot B_0$$

$$P_1 = A_1 \oplus B_1 \quad G_1 = A_1 \cdot B_1$$

2. step: Calculate bitwise Carry
Carry Logic

$$C_1 = G_0 + C_0 \cdot P_0$$

$$C_2 = G_1 + C_1 \cdot P_1 = G_1 + (G_0 + C_0 \cdot P_0) \cdot P_1 = G_1 + G_0 \cdot P_1 + C_0 \cdot P_0 \cdot P_1$$

$$C_3 = G_2 + G_1 \cdot P_2 + G_0 \cdot P_1 \cdot P_2 + C_0 \cdot P_0 \cdot P_1 \cdot P_2$$


Carry-Lookahead Adder

3. step: Calculate bitwise Sum
Sum Logic

$$S_0 = P_0 \oplus C_0$$

$$S_1 = P_1 \oplus C_1$$

Carry-Lookahead Adder

 


Task: Draw circuit of carry logic

Prof. Schumann

Digital System Design

95

Carry-Lookahead Adder

 

- Propagation delay for N-bit addition:

$$t_{\text{carry-lookahead}} \approx t_{\text{EXOR}} + t_{\text{AND}} + t_{\text{OR}} + t_{\text{EXOR}}$$

Propagation delay is almost independent of N (N≤32)!

Prof. Schumann

Digital System Design

96

Carry-Lookahead Adder

- But for cryptography $N=512$ or $N=2048$
- Carry logic is using N -input AND + N -input OR
- Gate delay of N -input AND/OR is function of N !

$$t_{\text{carry-lookahead}} \propto \log N$$

Optimistic approach, because distances signals have to travel on chip increase in proportion to N !

Tree Adder

- If lookahead is good, lookahead across lookahead!
- Many variations on tree adders
 - Brent-Kung
 - Sklansky
 - Kogge-Stone
 - etc.

Adder architectures offer area / power / delay tradeoffs.

Choose the best one for your application!

Multiplication

- Essential for μ P, DSP and graphic engines
- Example: `multiplcand_multiplier`

$$\begin{array}{r}
 \text{multiplicand} \quad \text{multiplier} \\
 1100 \times \underline{0101} : 12_{10} \times 5_{10} \\
 \begin{array}{r}
 1100 \\
 0000 \\
 1100 \\
 0000 \\
 \hline
 00111100 : 60_{10}
 \end{array}
 \end{array}$$

partial products

product

- M x N-bit multiplication
 - Produce N partial products (N rows), each have bit with M
 - Shift and sum these partial products to produce M+N-bit product

General Form

- Multiplicand: $Y = (y_{M-1}, y_{M-2}, \dots, y_1, y_0)$
- Multiplier: $X = (x_{N-1}, x_{N-2}, \dots, x_1, x_0)$

- **Product:**
$$P = \left(\sum_{j=0}^{M-1} y_j 2^j \right) \left(\sum_{i=0}^{N-1} x_i 2^i \right) = \sum_{i=0}^{N-1} \sum_{j=0}^{M-1} x_i y_j 2^{i+j}$$

[illegible]

Summing up the Partial Products

Two possible approaches of hardware implementation:

1. Add the first two rows of partial products by using a carry-propagate adder CPA (ripple-carry/carry-select/carry-lookahead). Use another CPA to add the third row of partial products and so forth. So we need $N-1$ adder for $M \times N$ -bit multiplication.


Summing up the Partial Products

Two possible approaches of hardware implementation:

2. Add the partial product to the result of the previous row using the carry-save redundant form! → use carry-save adders (CSA)

Finally convert the redundant form into a regular binary form! → use a carry-propagate adder (CPA)!

Approach 1: Array Multiplier with CPA

 


Prof. Schumann

Digital System Design

103

Approach 1: Array Multiplier with CPA

 First row can be simplified using AND-Gate only




Prof. Schumann

Digital System Design

104

Carry Save Addition (CSA)

 - A full adder sums 3 inputs and produces 2 outputs
- N full adders in parallel are called *carry save adder*
 - Produce N sums and N carry outs called the carry save redundant form output




Each N-bit CSA adds 3 words of N bit

$$t_{CSA} = \max(t_c, t_s)$$

Carry Save Addition (CSA)

Final sum can be calculated by:

 
1. Shifting the carry left by one place
2. Appending a 0 as most significant bit of the sums
3. Using a carry-ripple adder to add sums and carry outs together to produce N+1 bit final binary sum



CSA Application

- Multi input adder: K words
 - Use K-2 CSA
 - Use final CPA to compute actual result


Example: K=4

 

CSA Application

- M x N-bit Multiplication
 - Use N stages of CSAs (M full adder + AND-Gate)
 - Keep result in carry-save redundant form
 - Use final CPA to compute final result in binary form

Approach 2: Array Multiplier with CSA

 


Prof. Schumann

Digital System Design

109

Rectangular Array

 - Squash array to fit rectangular floorplan



Prof. Schumann

Digital System Design

110

Array Multiplier: Summary

- Both implementation approaches shows approx. same propagation delay (latency)!
- Notice that within the CSA array the full adder should have equally fast carry and sum propagation delay, because the greater of both limits the speed performance!
- Data flow within the CSA array is vertically only! So the array multiplier with CSA can be easily pipelined with the placement of registers between rows!

Advanced Multipliers

- Number of partial products can be reduced using a redundant number representation e.g. Booth-multiplier
- Try to transform serial operations into parallel operations to speed up the process of multiplication e.g. Wallace-tree
- Add sign extension: partial product can be negative