 




FPGA-based SoC Design

International Master of Science in Electrical Engineering

Prof. Dr. C. Jakob

University of Applied Sciences Darmstadt

h_da

Faculty of Electrical Engineering and Information Technology


fbeit

LFSRs – Basic Concepts and Applications

Today's Agenda

Intended topics for today's session

 - LFSRs – Basic Concepts and Applications
- LFSR for BIST and Test-Pattern Generation



LFSRs – Basic Concepts and Applications

International Master of Science in Electrical Engineering

Prof. Dr. C. Jakob

University of Applied Sciences Darmstadt

h_da

Faculty of Electrical Engineering and Information Technology

fbeit

LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design


LFSR Applications

- Test Pattern Generators and Output Response Analyzer (Built-in Self-Test (BIST))
- Counters
- Encryption
- Compression
- Checksums
- Generation of Pseudo-Random Bit Sequences (PRBS)

LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design

XOR based 4-bit Fibonacci LFSR

 

$$P(x) = x^4 + x^3 + 1$$

LFSR Fibonacci Configuration
(right shift operation)

Notes

- The all zero's state represents the lock-up state



Leonardo Fibonacci
1170-1240
(Image Source: wikipedia.com)

$$P(x) = x^4 + x^3 + 1$$

Characteristic Polynomial

Notes

- The characteristic polynomial is one way to describe an LFSR structure
- The polynomial is defined by the position of the XOR gates
- The degree of an LFSR polynomial is defined by its highest power and is equivalent to the number of flip-flops in the circuitry
- XOR feedback connection to the i^{th} FF is equivalent to the i^{th} coefficient
 - coefficient = 0 if no connection is present
 - coefficient = 1 if a connection is present
- There are two coefficients which are always included:
 - x^n degree of the polynomial and primary feedback
 - x^0 principle input to the shift register ...

LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design

XOR based 4-bit Fibonacci LFSR


Introduction to SystemVerilog

- Let's look at the generated output sequence ...

LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design

XOR based 4-bit Fibonacci LFSR

 

$$P(x) = x^4 + x^3 + 1$$

LFSR Fibonacci Configuration
(right shift operation)

$$P(x) = x^4 + x^3 + 1$$

Characteristic Polynomial

Notes

- An LFSR generates a pseudo random periodic sequence
- The maximum length of an n-bit LFSR sequence is:
 $2^n - 1$
- In case of an XOR based LFSR, the LFSR must start in a non-zero state, therefore the state sequence contains all possible bit patterns except the all 0s pattern
- The characteristic polynomial of an LFSR generating a maximum-length sequence is known as a **primitive polynomial** (more on that later)


Notes

- The all zero's state represents the lock-up state

LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design

XOR based 4-bit Fibonacci LFSR

 

Notes

- LFSR with the characteristic polynomial:

$$P(x) = x^4 + x^3 + 1$$

- Beginning in the all 1s state
- Maximum sequence length:

$$2^4 - 1 = 15$$

- Polynomial is primitive



Notes

- The all zero's state represents the lock-up state

LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design

XOR based 4-bit Fibonacci LFSR

  

Notes

- We are just starting at another position ...


LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design

XOR based 4-bit Fibonacci LFSR

```
1. module lfsr_fibonacci_4bit(  
2.     input logic clk, input logic reset_n,  
3.     output logic[3:0] q  
4. );  
5.  
6. logic feedback; assign feedback = q[0]^q[1];  
7.  
8. always_ff@(posedge clk)  
9.     if(reset_n == 0)  
10.         q <= 4'b1111;  
11.     else  
12.         q <= {feedback, q[3:1]};    // right-shift  
13.  
14. endmodule
```

1/1

 

[SystemVerilog] Source Code: lfsr_fibonacci_xor_4bit.sv

LFSRs – Basic Concepts and Applications


h_da – fbeit - FPGA-based SoC Design

XOR based 4-bit Fibonacci LFSR

```
1. module lfsr_fibonacci_4bit(  
2.     input logic clk, input logic reset_n,  
3.     output logic[3:0] q  
4. );  
5.  
6. logic feedback; assign feedback = q[0]^q[1];  
7.  
8. always_ff@(posedge clk)  
9.     if(reset_n == 0)  
10.        q <= 4'b1111;  
11.     else  
12.        q <= {feedback, q[3:1]};    // right-shift  
13.  
14. endmodule
```

1/1

 [SystemVerilog] Source Code: lfsr_fibonacci_xor_4bit.sv



LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design

Quiz

Notes

- By knowing the Fibonacci LFSR polynomial, we can easily sketch the corresponding circuitry ...


$$P(x) = x^8 + x^6 + x^5 + x^4 + 1$$

- How many taps?
- How many XOR gates?

8 taps (FF) ↑

$$P(x) = x^8 + x^6 + x^5 + x^4 + 1$$

↓ 3 XOR gates

 

LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design

What about LFSR's which are not based on a primitive polynomial?

Introduction to SystemVerilog

LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design

XOR based 4-bit Fibonacci LFSR

```
1. module lfsr_fibonacci_4bit(  
2.     input logic clk, input logic reset_n,  
3.     output logic[3:0] q  
4. );  
5. // non-primitive polynomial  
6. logic feedback; assign feedback = q[0]^q[2];  
7.  
8. always_ff@(posedge clk)  
9.     if(reset_n == 0)  
10.         q <= 4'b1111;  
11.     else  
12.         q <= {feedback,q[3:1]};    // right-shift  
13.  
14. endmodule
```

1/1

[SystemVerilog] Source Code: lfsr_fibonacci_xor_4bit.sv

LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design

XOR based 4-bit Fibonacci LFSR


```
1. module lfsr_fibonacci_4bit(  
2.     input logic clk, input logic reset_n,  
3.     output logic[3:0] q  
4. );  
5. // non-primitive polynomial  
6. logic feedback; assign feedback = q[0]^q[2];  
7.  
8. always_ff@(posedge clk)  
9.     if(reset_n == 0)  
10.        q <= 4'b1111;  
11.     else  
12.        q <= {feedback,q[3:1]}; // right-shift  
13.  
14. endmodule
```

1/1


[SystemVerilog] Source Code: lfsr_fibonacci_xor_4bit.sv

$$P(x) = x^4 + x^3 + 1 \rightarrow$$

$$P(x) = x^4 + x^2 + 1$$

 

 
Pseudo 'analog' representation of the discrete LFSR output



LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design

XOR based 4-bit Fibonacci LFSR

 

Notes

- Example LFSR with the characteristic polynomial:
 $P(x) = x^4 + x^2 + 1$
- Beginning in the all 1s state
- Maximum sequence length:
 $5 \neq 2^4 - 1 = 15$
- Polynomial is not primitive
- Non-primitive polynomials produce sequences
 $< 2^n - 1$

Notes

- The all zero's state represents the lock-up state

LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design

LFSR circuits can also be built equivalently with XNOR states ...



Introduction to SystemVerilog

- LFSR circuits can also be built equivalently with **XNOR** gates, with the lock state being all '1's instead of all '0's.

LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design

XNOR based 4-bit Fibonacci LFSR

  

Notes

- The all **one's state** represents the lock-up state

LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design

XNOR based 4-bit Fibonacci LFSR

```
1. module lfsr_fibonacci_4bit(  
2.     input logic clk, input logic reset_n,  
3.     output logic[3:0] q  
4. );  
5. // XNOR based feedback-function  
6. logic feedback; assign feedback = q[0]~^q[1];  
7.  
8. always_ff@(posedge clk)  
9.     if(reset_n == 0)  
10.         q <= 4'b1001;  
11.     else  
12.         q <= {feedback,q[3:1]}; // right-shift  
13.  
14. endmodule
```

1/1

[SystemVerilog] Source Code: lfsr_fibonacci_xor_4bit.sv



LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design

XNOR based 4-bit Fibonacci LFSR

```
1. module lfsr_fibonacci_4bit(  
2.     input logic clk, input logic reset_n,  
3.     output logic[3:0] q  
4. );  
5. // XNOR based feedback-function  
6. logic feedback; assign feedback = q[0]~^q[1];  
7.  
8. always_ff@(posedge clk)  
9.     if(reset_n == 0)  
10.         q <= 4'b1001;  
11.     else  
12.         q <= {feedback,q[3:1]}; // right-shift  
13.  
14. endmodule
```

1/1


[SystemVerilog] Source Code: lfsr_fibonacci_xor_4bit.sv

$$P(x) = x^4 + x^3 + 1 \longrightarrow$$

LFSR Fibonacci **XOR** Configuration

$$P(x) = x^4 + x^3 + 1$$

LFSR Fibonacci **XNOR** Configuration

 

Pseudo 'analog' representation of the discrete LFSR output

LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design

Something in between - Why are XOR or XNOR operations linear operations?

Introduction to SystemVerilog

Why are XOR or XNOR operations linear operations?

- In case of a Boolean XOR/XNOR function, the state change of one input is always causing an output change, independent of the fixed state of the other input.
- If you compare all 6 binary operations, you'll see, that this property doesn't apply for AND, OR, NAND, NOR but is valid for **XOR** - and **XNOR** operations ...

LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design


Galois LFSR Structures ...?

Introduction to SystemVerilog

LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design

XOR based 4-bit Fibonacci LFSR

 

$$P(x) = x^4 + x^3 + x^2 + 1$$

LFSR Fibonacci Configuration
(right shift operation)

$$P(x) = x^4 + x^3 + x^2 + 1$$

Characteristic Polynomial

Notes

- One way of implementing LFSRs; all XOR gates are fed sequentially into one another and end up as the input to the most significant bit of the LFSR. **Simply put, the XORs are external from the shift register.**

Notes

- The all zero state represents the lock-up state

Fibonacci / Galois conversion

- For a given Fibonacci LFSR, described by the polynomial $P(x)$, the corresponding Galois LFSR representation

Notes

- Assume the following Fibonacci LFSR polynomial

$$P(x) = x^4 + x^3 + x^2 + 1$$

- In order to convert this polynomial to an equivalent Galois representation, adapt the respective exponents as follows

$$P(x) = x^{4-4} + x^{4-3} + x^{4-2} + x^{4-0}$$

$$P(x) = x^0 + x^1 + x^2 + x^4$$


- Rearranging the previous expression leads to

$$P(x) = x^4 + x^2 + x^1 + x^0 = x^4 + x^2 + x^1 + 1$$

LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design

XOR based 4-bit Galois LFSR

 

$$P(x) = x^4 + x^2 + x^1 + 1$$

Characteristic Polynomial

Notes

- Another way to implement an LFSR is to place the XOR gates inside the shift register. This alternate structure generates an output stream with identical sequence length



Évariste Galois , 1811-1832
(Image Source: wikipedia.com)

What's the advantage of a Galois LFSR structure?

LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design

XOR based 4-bit Galois LFSR


```
1. module lfsr_galois_4bit(  
2.     input logic clk, input logic reset_n,  
3.     output logic[3:0] q  
4. );  
5.  
6. always_ff@(posedge clk)  
7.     if(reset_n == 0)  
8.         q <= 4'b1001;  
11.    else  
12.        q <= {q[0],q[3]^q[0],q[2]^q[0],q[1]};  
13.  
14. endmodule
```

1/1

[SystemVerilog] Source Code: lfsr_galois_4bit.sv

$$P(x) = x^4 + x^2 + x^1 + 1$$

Galois LFSR Configuration

 

Pseudo 'analog' representation of the discrete LFSR output

LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design



Fibonacci vs. Galois LFSR sequences ...

FPGA based System Design

LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design

XOR based 4-bit Fibonacci LFSR

  

$$P(x) = x^4 + x^3 + x^2 + 1$$

Fibonacci LFSR Polynomial

Seed

0	0	1	1	3
0	0	0	1	1
1	0	0	0	8
0	1	0	0	4
1	0	1	0	10
1	1	0	1	13
0	1	1	0	6

7

$$P(x) = x^4 + x^2 + x^1 + 1$$

Galois LFSR Polynomial

Seed

0	0	1	1	3
1	1	1	1	15
1	0	0	1	9
1	0	1	0	10
0	1	0	1	5
1	1	0	0	12
0	1	1	0	6

7

Notes

- Non-primitive polynomials
- The output sequences are different, however they've got the same sequence-length

LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design

XOR based 4-bit Galois LFSR

```
1. module lfsr_galois_4bit(  
2.     input logic clk, input logic reset_n,  
3.     output logic[3:0] q  
4. );  
5.  
6. always_ff@(posedge clk)  
7.     if(reset_n == 0)  
8.         q <= 4'b1001;  
11.    else  
12.        q <= {q[0],q[3]^q[0],q[2]^q[0],q[1]};  
13.  
14. endmodule
```

1/1

[SystemVerilog] Source Code: lfsr_galois_4bit.sv


$$P(x) = x^4 + x^3 + x^2 + 1$$

Fibonacci LFSR Polynomial



$$P(x) = x^4 + x^2 + x^1 + 1$$

Galois LFSR Configuration

 

Pseudo 'analog' representation of the discrete LFSR output

LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design

How to know if a LFSR polynomial is a primitive polynomial?

FPGA based System Design

LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design

Primitive LFSR polynomials with minimum number of XOR gates ...

Bits	Polynomial	Period	Notes
2	$P(x) = x^2 + x + 1$	3	- The following table lists maximal-length polynomials for shift-register lengths up to 11. Note that more than one maximal-length polynomial may exist for any given shift-register length. - A list of alternative maximal-length polynomials for various shift-register lengths can be found in www.xilinx.com/support/documentation/application_notes/xapp052.pdf
3	$P(x) = x^3 + x^2 + 1$	7	
4	$P(x) = x^4 + x^3 + 1$	15	
5	$P(x) = x^5 + x^3 + 1$	31	
6	$P(x) = x^6 + x^5 + 1$	63	
7	$P(x) = x^7 + x^6 + 1$	127	
8	$P(x) = x^8 + x^6 + x^5 + x^4 + 1$	255	
9	$P(x) = x^9 + x^5 + 1$	511	... 153 $P(x) = x^{153} + x^{152} + 1$ $2^{153} - 1$ If this LFSR operates at 50MHz, the sequence first repeats after 72412363912022317658969354107027 years ...
10	$P(x) = x^{10} + x^7 + 1$	1023	
11	$P(x) = x^{11} + x^9 + 1$	2047	


LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design

How to measure the sequence length of an LFSR?

FPGA based System Design

 Computing the auto-correlation function of an LFSR reveals its sequence length ...



Notes

- The discrete auto-correlation function of an N-sample input sequence is defined as:

$$r_{xx}[k] = \sum_{n=0}^{N-1} x[n]x[n-k]$$

- where in hardware, the delays $x[n-k]$ can be implemented using registers, i.e., a delay line containing earlier samples, hence the minus sign in front of k .
- The auto-correlation response is symmetric about the zeroth lag, so in a hardware implementation only the zeroth and positive samples of the autocorrelation need to be calculated
- LFSR degree?

LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design

How to include the lock-up state into the regular state sequence of an XOR based Fibonacci LFSR ...

FPGA based System Design

LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design

First Solution

FPGA based System Design


LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design

How to include the lock-up state into the regular state sequence ...

First solution

Linear Feedback Shift Register

 

Seed	0	0	1	1	3
'Lock-up' State	0	0	0	1	1
State	0	0	0	0	0
	1	0	0	0	8
	0	1	0	0	4
	0	0	1	0	2
	1	0	0	1	9
	1	1	0	0	12
	0	1	1	0	6
	1	0	1	1	11
	0	1	0	1	5
	1	0	1	0	10
	1	1	0	1	13
	1	1	1	0	14
	1	1	1	1	15
	0	1	1	1	7
	0	0	1	1	3
	0	0	0	1	1

16

LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design

XOR based 4-bit extended Fibonacci LFSR

```
1. module ext_lfsr_fibonacci_4bit_comp(
2.     input logic clk, input logic reset_n,
3.     output logic[3:0] q
4. );
5. logic lock;
6. assign lock = ((q == 0) || (q == 1)) ? 1 : 0;
7. logic feedback; assign feedback = q[0]^q[1]^lock;
8.
9. always_ff@(posedge clk)
10.    if(reset_n == 0)
11.        q <= 4'b1101;
12.    else
13.        q <={feedback, q[3:1]};
14.
15. endmodule
```

1/1

$$P(x) = x^4 + x^3 + 1$$

LFSR Fibonacci Configuration



Pseudo 'analog' representation of the discrete LFSR output

[SystemVerilog] Source Code: ext_lfsr_fibonacci_4bit_comp.sv

LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design

Second Solution

FPGA based System Design

LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design

How to include the lock-up state into the regular state sequence ...

Second solution ...

Linear Feedback Shift Register

Notes

- The all '0's state can't be entered during normal operation but we can get close:

0 0 0 1₁

- We know that this is a legal state since the only illegal state is all 0's. If the first 3 bits are '0', then bit 0 must be a '1'.
- Now, since the XOR inputs are a function of taps, including the bit 0 tap, we know what the output of the XOR function will be! It must be a '1'. So normally the next state will be:

1 0 0 0₈

$$P(x) = x^4 + x^3 + 1$$

LFSR Fibonacci Configuration
(right shift operation)

LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design

How to include the lock-up state into the regular state sequence ...

Second solution ...

Linear Feedback Shift Register

Notes

- So, in order to include the actual illegal lock-up state, start with detecting the “**almost**” lock-up state:

0 0 0 x

- Computing the Boolean NOR function for the first three will provide a ‘1’ when they are all ‘0’. We add this term to the regular XOR feedback function ...


$$P(x) = x^4 + x^3 + 1$$

LFSR Fibonacci Configuration
[right shift operation]

LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design

Extended XOR based 4-bit Fibonacci LFSR

 

$$P(x) = x^4 + x^3 + 1$$

LFSR Fibonacci Configuration
(right shift operation)

Notes

- The NOR gate generates a logic high output only for an all-zero input.
- This only applies for the input patterns $q = 4'b0000$ and $4'b0001$.
- In the present case, the output of the NOR gate acts as a control signal:


ctrl	d	q
0	0	0
0	1	1

ctrl	d	q
1	0	1
1	1	0

- For ctrl being low, the input signal d is just passed to the output q, whereas when ctrl is high, the input is inverted and passed to the output.
- The XOR gate therefore acts as an inverter that can be activated or deactivated.

h_da – fbeit - FPGA-based SoC Design

Extended XOR based 4-bit Fibonacci LFSR

 

Seed	0	0	1	1	3
	0	0	0	1	1
	0	0	0	0	0
	1	0	0	0	8
	0	1	0	0	4
	0	0	1	0	2
	1	0	0	1	9
	1	1	0	0	12
	0	1	1	0	6
	1	0	1	1	11
	0	1	0	1	5
	1	0	1	0	10
	1	1	0	1	13
	1	1	1	0	14
	1	1	1	1	15
	0	1	1	1	7
	0	0	1	1	3
	0	0	0	1	1

LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design

XOR based 4-bit extended Fibonacci LFSR


```
1. module lfsr_galois_4bit_nor(
2.     input logic clk, input logic reset_n,
3.     output logic[3:0] q
4. );
5.
6. logic tmp;      assign tmp      = ~(q[1]|q[2]|q[3]);
7. logic feedback; assign feedback = q[0]^q[1]^tmp;
8.
9. always_ff@(posedge clk)
10.    if(reset_n == 0)
11.        q <= 4'b1101;
12.    else
13.        q <={feedback,q[3:1]};
14.
15. endmodule
```

1/1

[SystemVerilog] Source Code: ext_lfsr_fibonacci_4bit_nor.sv

$$P(x) = x^4 + x^3 + 1$$

LFSR Fibonacci Configuration

 

Pseudo 'analog' representation of the discrete LFSR output

LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design


How to include the lock-up state into the regular state sequence of an XNOR based Fibonacci LFSR ...

FPGA based System Design

LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design

Extended XNOR based 4-bit Fibonacci LFSR

 

$$P(x) = x^4 + x^3 + 1$$

LFSR Fibonacci Configuration
(right shift operation)

Notes


- Now, the all **one's state** represents the lock-up state.
- The NAND gate generates a logic high output only for an all-ones input.
- This only applies for the input patterns $q = 4'b1110$ and $4'b1111$.
- In the present case, the output of the NAND gate acts as a control signal:

ctrl	d	q	ctrl	d	q
0	0	1	1	0	0
0	1	0	1	1	1

- For ctrl being low, the input signal d is inverted and passed to the output q, whereas when ctrl is high, the input is just passed to the output.
- The XNOR gate therefore acts as an inverter that can be activated or deactivated.

h_da – fbeit - FPGA-based SoC Design

Extended XNOR based 4-bit Fibonacci LFSR

 

Seed	0	0	1	1	
	0	0	1	1	3
	0	0	0	1	1
	0	0	0	0	0
	1	0	0	0	8
	0	1	0	0	4
	0	0	1	0	2
	1	0	0	1	9
	1	1	0	0	12
	0	1	1	0	6
	1	0	1	1	11
	0	1	0	1	5
	1	0	1	0	10
	1	1	0	1	13
	1	1	1	0	14
	1	1	1	1	15
'Lock-up' State	0	1	1	1	7
	0	0	1	1	3
	0	0	0	1	1

LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design


How to include the lock-up state into the regular state sequence of an XOR/XNOR based Galois LFSRs ...

FPGA based System Design


LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design

XOR based 4-bit Galois LFSR

 

XNOR based 4-bit Galois LFSR

 

LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design


LFSR's in Dual Clock (DC) First in First Out (FIFO) Memories ...

FPGA based System Design

LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design

 LFSR's in Single Clock (SC) First in First Out (FIFO) memories



- Address pointers are used internally to keep the next write and read position within the dual-port memory
- Advantage of using an LFSR counter?
- If both pointers have the same values after a write operation, the FIFO is full

LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design


Configurable LFSR structure ...

FPGA based System Design

LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design

Configurable LFSR structure ...

 

$$P(x) = x^8 + c_7x^7 + c_6x^6 + c_5x^5 + c_4x^4 + c_3x^3 + c_2x^2 + c_1x^1 + 1$$

LFSR Fibonacci Configuration
(right shift operation)

LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design


LFSRs as Pseudo Random Number Generators (PRNG)

FPGA based System Design

LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design

 LFSRs as Pseudo Random Number Generators (PRNG)



Pseudo 'analog' representation of the discrete LFSR output

Notes

- For what type of applications, pseudo random numbers are not sufficient any more and why?

LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design


LFSRs as Pseudo Random Number Generators (PRNG) with predefined distribution

FPGA based System Design

LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design

 LFSRs as Pseudo Random Number Generators (PRNG) with predefined distribution




Notes

- Linear Feedback Shift Registers produce a sequence of numbers that appears to be uniformly distributed over the range 1 to $2^n - 1$, where n is the LFSR size. For this type of generator, each output value has an **equal probability of appearing (uniform distribution)**.

 Question

- So I know how to generate a uniform random variable. How do I generate others?

LFSRs as Pseudo Random Number Generators (PRNG) with predefined distribution





Notes

- Some applications require the generation of random numbers that aren't uniformly distributed. In many DSP applications, it is often necessary to produce values that are **normally distributed**. One of the most popular schemes to generate normal distributed pseudo random numbers is based on the Central Limit Theorem (CLT).
- In probability theory, the **Central Limit Theorem CLT** states that, given certain conditions, the arithmetic mean of a sufficiently large number of iterates of independent and identically distributed random variables will be approximately normally distributed. Or in other words: The sum of N random numbers will approach a normal distribution as N approaches infinity.
- Once we can generate pseudo random sequences with normal distribution, we can also adjust the **signal's mean** and **variance** to use it for any purpose.


LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design

  LFSRs as Pseudo Random Number Generators (PRNG) with predefined distribution



 LFSRs as Pseudo Random Number Generators (PRNG) with predefined distribution



Notes

- Consider an **exponential distribution**: the density of an exponential random variable X is given by

$$f_X(x) = \begin{cases} e^{-x} & x \geq 0 \\ 0 & x < 0. \end{cases}$$

- Thus, its **distribution function** is given by

$$F_X(x) = 1 - e^{-x}$$

- Let us determine the **inverse to** $F_X(x)$. We need to solve for x in

$$1 - e^{-x} = u$$


- Thus,

$$x = -\log(1 - u)$$

LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design

 LFSRs as Pseudo Random Number Generators (PRNG) with predefined distribution



LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design

Built-In Self-Test (BIST) - Generating bit streams with defined bit probabilities

FPGA based System Design

Transforming Bit Probabilities with Combinational Logic

- The intention is to generate bit sequences with random bit density.
- We are using LFSRs in conjunction with combinational logic circuits to transform bit streams with given source probabilities into bit streams with different target probabilities.

LFSRs – Basic Concepts and Applications


h_da – fbeit - FPGA-based SoC Design

Transforming Bit Probabilities with Combinational Logic

Here, the probabilities of obtaining a one in the input streams is 0.4.

1 0 1 0 0 0 1 0 0 1

$$P_0 = 0.4$$

 

0 1 0 1 1 1 0 1 1 0

$$P_q = 0.6$$

Here, the probabilities of obtaining a one in the output streams is 0.6.


Notes

- With probability p , we mean “with a probability of p being at logic one”.
- Given an input with probability 0.4, an inverter will have an output z with probability 0.6 since: $P_q = 1 - P_0$

LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design

 Transforming Bit Probabilities with Combinational Logic




Notes

- With probability p , we mean “with a probability of p being at logic one”
- **Homework:** Derive the upper equation for a logical OR gate

LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design

 Transforming Bit Probabilities with Combinational Logic




Notes

- With probability p , we mean “with a probability of p being at logic one”

LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design

 Generating bit streams with defined bit probabilities




	q_3	q_2	q_1	q_0	
Seed	0	0	1	1	3
'Lock-up' State	0	0	0	1	1
	0	0	0	0	0
	1	0	0	0	8
	0	1	0	0	4
	0	0	1	0	2
	1	0	0	1	9
	1	1	0	0	12
	0	1	1	0	6
	1	0	1	1	11
	0	1	0	1	5
	1	0	1	0	10
	1	1	0	1	13
	1	1	1	0	14
	1	1	1	1	15
	0	1	1	1	7

16

At every
output stage:
 $8 \times 1 \ \& \ 8 \times 0$

$$P(q_x = 1) = 0.5$$

 

LFSRs – Basic Concepts and Applications

h_da – fbeit - FPGA-based SoC Design

How to test these structures?

FPGA based System Design