

Amplifier: 4th order Bandpass and How to Derive the Design Parameters

SDHD

18.04.2023

Prof. Dr.-Ing. Stephan Bannwarth

Agenda

- Which Parameters do we need for the Amplifier Design?
- Derivation of the Parameters
- Design of our Amplifier

Needed Parameters

- Bandpass: Amplification
- Bandpass: corner frequencies

Depending on

Max./Min. input
amplitude and
Max./Min. output
amplitude

Speed of the
Movement

Task to do

Study your
datasheet

Initial
Measurnment on a
sample

Derivation from
theory

Simulation

Doppler Shift
calculations

- Modul (IPM-165) datasheet

Schematic Capture: Amplifier: 4th order Bandpass

